

Title: Quantum Information Lecture - 230322

Speakers: Eduardo Martin-Martinez

Collection: Quantum Information (2022/2023)


Date: March 22, 2023 - 9:00 AM

URL: <https://pirsa.org/23030010>

Classical Logic

NOT

in	out
0	1
1	0

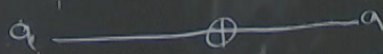

OR

in		out	
a	b	a	aORb
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	1

NAND

in		out	
a	b	a	aNANDb
0	0	0	1
0	1	0	1
1	0	1	1
1	1	1	0

NOR


in		out	
a	b	a	aNORb
0	0	0	1
0	1	0	0
1	0	1	0
1	1	1	0

AND

in		out	
a	b	a	a·b
0	0	0	0
0	1	0	0
1	0	0	0
1	1	1	1

XOR (CNOT)

in		out	
a	b	a	a⊕b
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

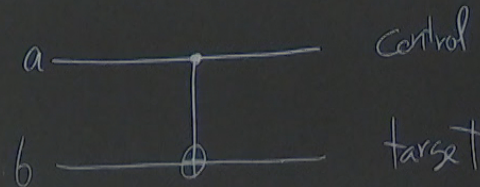


NAND

in	a	b	out a NAND b
0	0	0	1
0	0	1	1
0	1	0	1
1	1	1	0

NOR

in		out	
a	b	a	a NOR b
0	0	0	1
0	1	0	0
1	0	0	0
1	1	0	0

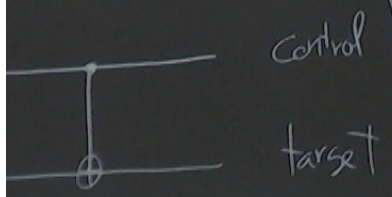

TOFFOLI (Doubly controlled Not)

in			out		
a	b	c	a	b	$c \oplus a \cdot b$
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	1	1	1
1	1	1	1	1	0

controlled Not)

Universal set of gates

A set of gates is universal if it can be used to build any functions

$$f: \mathbb{Z}_2^n \rightarrow \mathbb{Z}_2^m \quad f(x_1, \dots, x_n) = (x'_1, \dots, x'_m)$$

e.g. {XOR, AND} is universal

z' {NOT, AND}

{NAND}

{TOFFOLI}

$$a \oplus b = a \text{ XOR } b = (a \text{ AND } (\text{Not } b)) \text{ OR } ((\text{Not } a) \text{ AND } b)$$

$$a \text{ OR } b = a \cdot b \oplus a \oplus b = \text{Not} (\text{Not } a \text{ AND } \text{Not } b)$$

$$\text{Not } a = (a \text{ NAND } a)$$

$$a \text{ AND } b = (a \text{ NAND } b) \text{ NAND } (a \text{ NAND } b)$$

Classical Logic

NOT (R)

in	out
0	1
1	0



OR

in		out	
a	b	a	aORb
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	1

NAND

in		out	
a	b	a	aNANDb
0	0	0	1
0	1	0	1
1	0	1	1
1	1	1	0

NOR


in		out	
a	b	a	aNORb
0	0	0	1
0	1	0	0
1	0	1	0
1	1	1	0

AND

in		out	
a	b	a	a&b
0	0	0	0
0	1	0	0
1	0	0	0
1	1	1	1

XOR (CNOT) (R)

in		out	
a	b	a	a&^b
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

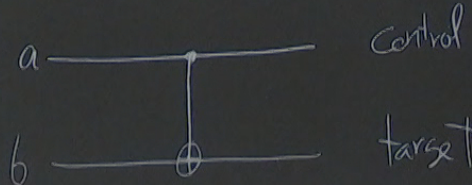

(R) TOP

a	b	a	b
0	0	0	0
0	1	0	1
1	0	1	0
1	1	1	1

$(\text{Not } b) \text{ OR } ((\text{Not } a) \text{ AND } b)$

$(\text{Not } a \text{ AND } \text{Not } b)$


$(a \text{ NAND } b)$

$$\text{NOT } a = a \text{ NOR } a$$

$$a \text{ AND } b = (a \text{ NOR } a) \text{ NOR } (b \text{ NOR } b)$$

$$a \text{ NAND } b = \text{TOFFOLI}(a, b, 1)$$


2-bit ADDER

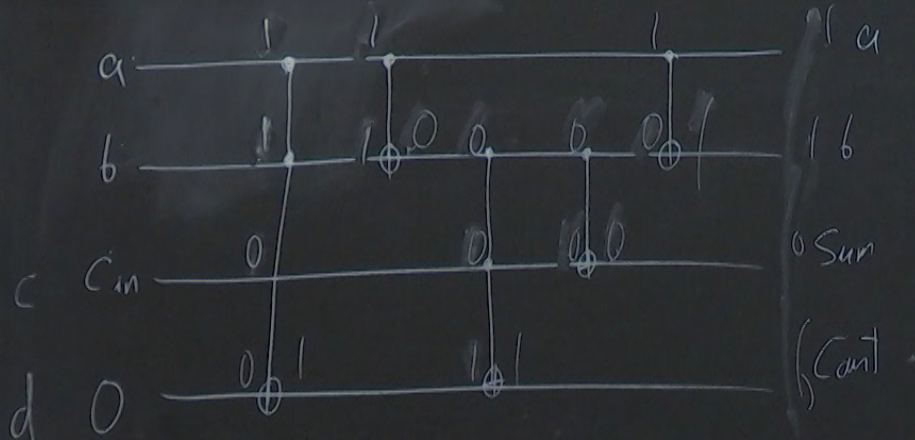


in				out			
a	b	c	d	a	b	Sum	Cont
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	1	0
		⋮					
1	1	0	0	1	1	0	1

Single qubit gates


Pauli Gates

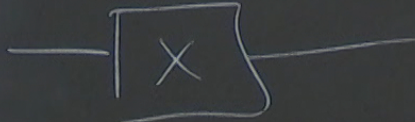
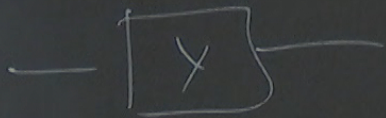
$$\hat{\sigma}_x, \text{NOT} \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix}$$


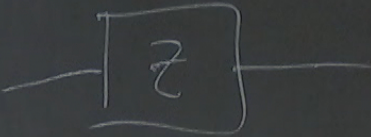
$$\hat{\sigma}_y \begin{pmatrix} 0 & -i \\ i & 0 \end{pmatrix}$$




$$\hat{\sigma}_z \begin{pmatrix} 1 & 0 \\ 0 & -1 \end{pmatrix}$$

$$|0\rangle = \begin{pmatrix} 1 \\ 0 \end{pmatrix}$$

$$|1\rangle = \begin{pmatrix} 0 \\ 1 \end{pmatrix}$$

$$|\psi\rangle =$$

Hadamard gate

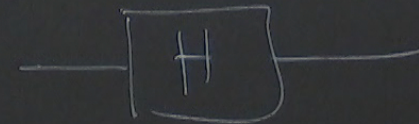


$$\frac{1}{\sqrt{2}} \begin{pmatrix} 1 & 1 \\ 1 & -1 \end{pmatrix}$$

$$\begin{pmatrix} |1\rangle \\ |0\rangle \\ |1\rangle \end{pmatrix}$$

$$|\psi\rangle = \alpha |0\rangle + \beta |1\rangle \rightarrow \begin{pmatrix} \alpha \\ \beta \end{pmatrix}$$


Hadamard gate

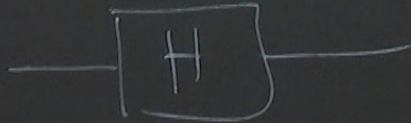


$$\frac{1}{\sqrt{2}} \begin{pmatrix} 1 & 1 \\ 1 & -1 \end{pmatrix}$$

$$|0\rangle \rightarrow \frac{1}{\sqrt{2}} (|0\rangle + |1\rangle) \equiv |+\rangle$$

$$|1\rangle \rightarrow \frac{1}{\sqrt{2}} (|0\rangle - |1\rangle) \equiv |-\rangle$$

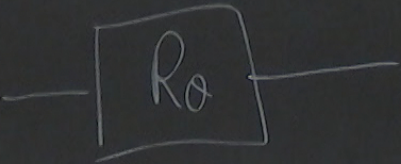
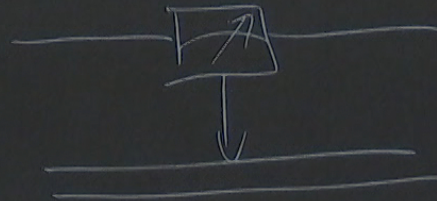
$$\begin{pmatrix} 1 & 0 \\ 0 & e^{i\alpha} \end{pmatrix}$$




→

$$|1\rangle \rightarrow \begin{pmatrix} \alpha \\ \beta \end{pmatrix}$$

$$|0\rangle \rightarrow \frac{1}{\sqrt{2}} (|0\rangle + |1\rangle) \equiv |+\rangle$$

$$|1\rangle \rightarrow \frac{1}{\sqrt{2}} (|0\rangle - |1\rangle) \equiv |-\rangle$$

classically controlled NOT

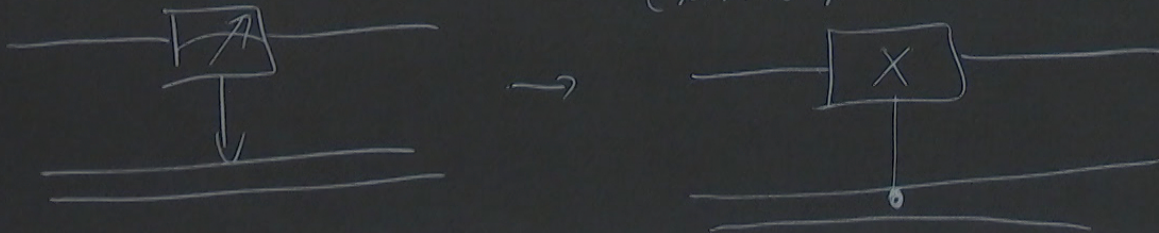


$|00\rangle \rightarrow |00\rangle$
 $|01\rangle \rightarrow |01\rangle$
 $|10\rangle \rightarrow |11\rangle$
 $|11\rangle \rightarrow |10\rangle$

$$\begin{pmatrix} I_2 & 0 \\ 0 & \sigma_x \end{pmatrix}$$

$|00\rangle = |0\rangle \otimes |0\rangle \approx \begin{pmatrix} 1 \\ 0 \\ 0 \\ 0 \end{pmatrix}$
 $|01\rangle = |0\rangle \otimes |1\rangle \rightarrow \begin{pmatrix} 0 \\ 1 \\ 0 \\ 0 \end{pmatrix}$
 $|10\rangle = |1\rangle \otimes |0\rangle \rightarrow \begin{pmatrix} 0 \\ 0 \\ 1 \\ 0 \end{pmatrix}$
 $|11\rangle = |1\rangle \otimes |1\rangle \rightarrow \begin{pmatrix} 0 \\ 0 \\ 0 \\ 1 \end{pmatrix}$


TWO QUBIT GATES

THREE CNOT $|a\ b\rangle \rightarrow |a\ a\oplus b\rangle$

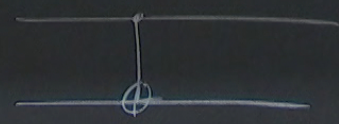


$|00\rangle \rightarrow |00\rangle$
 $|01\rangle \rightarrow |01\rangle$
 $|10\rangle \rightarrow |11\rangle$
 $|11\rangle \rightarrow |10\rangle$

TOFFOLI : $|a\ b\ c\rangle \rightarrow |a\ b\ c\oplus a\cdot b\rangle$

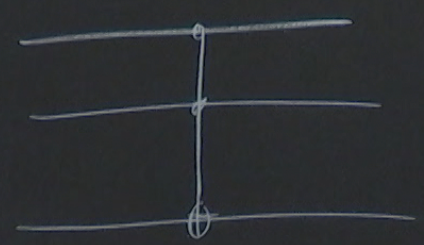

$$\begin{pmatrix} H_3 & & \\ & H_3 & \\ & & \sigma_x \end{pmatrix}$$

SWAP

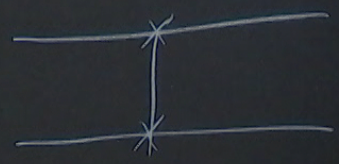

$a \begin{pmatrix} \alpha_1 \\ \beta_1 \end{pmatrix}$
 $b \begin{pmatrix} \alpha_2 \\ \beta_2 \end{pmatrix}$

$$\begin{aligned}
 |00\rangle &= |0\rangle \otimes |0\rangle \approx \begin{pmatrix} 1 \\ 0 \\ 0 \\ 0 \end{pmatrix} \\
 |01\rangle &= |0\rangle \otimes |1\rangle \longrightarrow \begin{pmatrix} 0 \\ 1 \\ 0 \\ 0 \end{pmatrix} \\
 |10\rangle &= |1\rangle \otimes |0\rangle \longrightarrow \begin{pmatrix} 0 \\ 0 \\ 1 \\ 0 \end{pmatrix} \\
 |11\rangle &= |1\rangle \otimes |1\rangle \longrightarrow \begin{pmatrix} 0 \\ 0 \\ 0 \\ 1 \end{pmatrix}
 \end{aligned}$$

$$\begin{pmatrix} \alpha_2 \\ \beta_2 \\ \alpha_1 \\ \beta_1 \end{pmatrix}
 \begin{pmatrix}
 1 & 0 & 0 & 0 \\
 0 & 0 & 1 & 0 \\
 0 & 1 & 0 & 0 \\
 0 & 0 & 0 & 1
 \end{pmatrix}$$

