

Title: Quantum Information Lecture

Speakers: Eduardo Martin-Martinez

Collection: Quantum Information 2023/24


Date: March 20, 2024 - 9:00 AM

URL: <https://pirsa.org/24030059>

Classical Logic


$$\text{NOT } A \equiv A'$$

Input A	NOT A
0	1
1	0

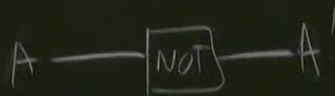


$$A \text{ OR } B \equiv A + B$$

Input		Output	
A	B	A	A OR B
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	1

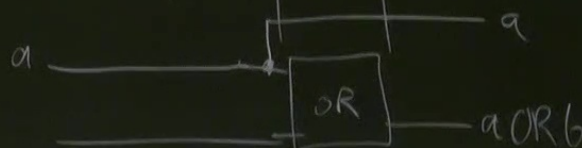

$$A \text{ AND } B \equiv A \cdot B$$

Input		Output	
A	B	A	A AND B
0	0	0	0
0	1	0	0
1	0	0	0
1	1	1	1

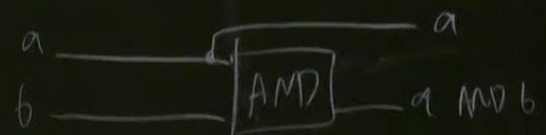

$$A \text{ NOR } B \equiv (A+B)'$$


Input		output	
A	B	A	A NOR B
0	0	0	1
0	1	0	0
1	0	1	0
1	1	1	0

$$A \text{ NAND } B \equiv A \oplus B$$

Input		output	
A	B	A	A NAND B
0	0	0	1
0	1	0	1
1	0	1	1
1	1	1	0


$$A \text{ XOR } B \equiv A \oplus B \quad / \text{CNOT}$$

Input		Output	
A	B	A	A XOR B
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

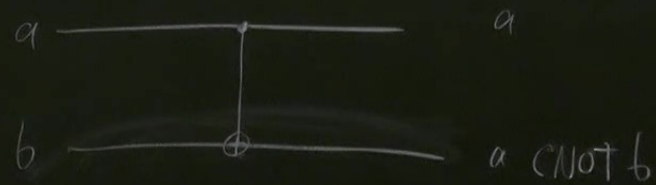

$$T_{\text{OFFOLI}}(A, B, C) = C \oplus A \cdot B = C \text{CNOT}$$

Input			Output		
A	B	C	A	B	$C \oplus A \cdot B$
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	1	1	0
1	1	1	1	1	1

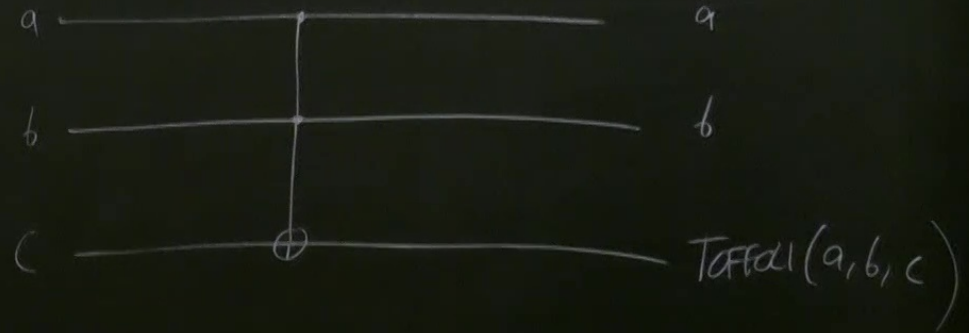

Universal set of gates

A set of gates is universal if it can be used to build any function $f: Z_2^n$

$$f(x_1, \dots, x_n) = (x_1', \dots, x_n')$$

Example \rightarrow of Universal sets: $\{AND, OR, NOT\}$, $\{AND, NOT\}$, $\{XOR, NOT\}$

Examples of equivalence XOR from $\{AND, OR, NOT\} \Rightarrow a XOR b = (a AND (NOT b))$

OR from $\{AND, NOT\} \Rightarrow a OR b = NOT((NOT a) AND (NOT b))$

Universal set of gates

A set of gates is universal if it can be used to build any function $f: \mathbb{Z}_2^n \rightarrow \mathbb{Z}_2^m$

$$f(x_1, \dots, x_n) = (x'_1, \dots, x'_m)$$

Example \rightarrow of Universal sets: $\{AND, OR, NOT\}$, $\{AND, NOT\}$, $\{XOR, NOT\}$

Examples of equivalence XOR from $\{AND, OR, NOT\} \Rightarrow a XOR b = (a AND (NOT b)) OR ((NOT a) AND b)$

OR from $\{AND, NOT\} \Rightarrow a OR b = NOT((NOT a) AND (NOT b))$

OR from $\{AND, XOR\} \Rightarrow a OR b = (a AND b) XOR (a XOR b)$

be used to build any function $f: \mathbb{Z}_2^n \rightarrow \mathbb{Z}_2^m$ $n, m \in \mathbb{Z}^+$ $m \leq n$

$\{OR, NOT\}$, $\{AND, NOT\}$, $\{XOR, AND\}$, $\{NAND\}$, $\{NOR\}$, $\{TOFFOLI\}$

$$\{OR, NOT\} \Rightarrow a XOR b = (a AND (NOT b)) OR ((NOT a) AND b)$$

$$(a AND (NOT b))$$


$$b XOR (a XOR b)$$

$$\text{OR from } \{\text{AND, XOR}\} \Rightarrow a \text{ OR } b = (a \text{ AND } b) \text{ XOR } (a \text{ XOR } b)$$

$$\text{NOT from } \{\text{NAND}\} \Rightarrow \text{NOT } a = a \text{ NAND } a$$


$$\text{AND from } \{\text{NAND}\} \Rightarrow a \text{ AND } b = (a \text{ NAND } b) \text{ NAND } (a \text{ NAND } b)$$
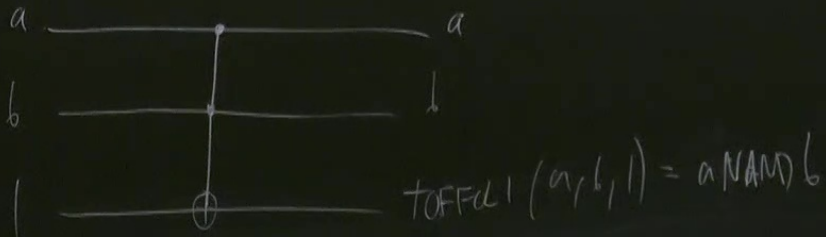
$$\text{NAND from } \{\text{TOFFOLI}\} \Rightarrow a \text{ NAND } b = \text{NOT}(a \text{ AND } b) = (1) \text{ CNOT}(a \text{ AND } b) = \text{TOFFOLI}(a, b, 1)$$




$$\text{Toffoli}(A, B, C) = C \oplus A \cdot B = C \text{ NOT}$$


Input			Output		
A	B	C	A	B	$C \oplus A \cdot B$
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	1	1	0
1	1	1	1	1	1

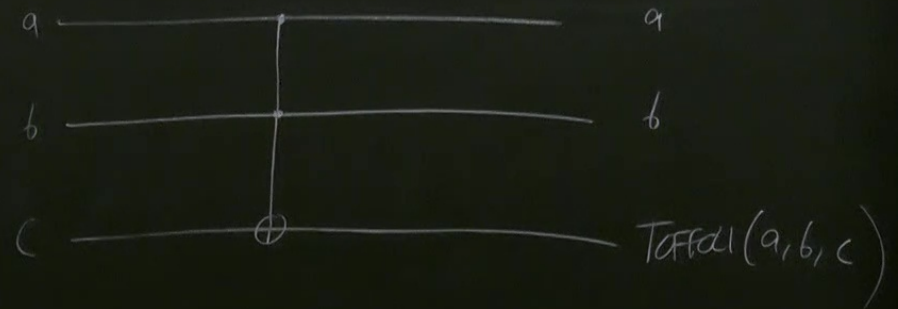

$$A \text{ XOR } B \equiv A \oplus B \quad / \text{CNOT}$$

Input		Output	
A	B	A	A XOR B
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

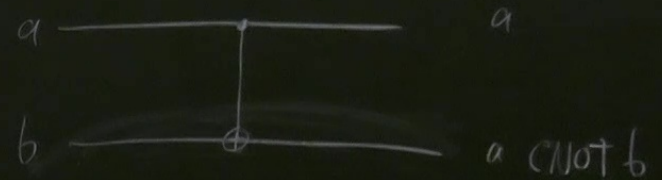

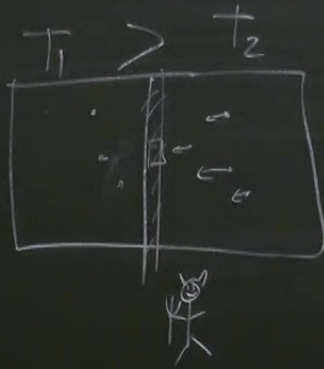

Two-bit adder

Input				Output			
a	b	Cin	d	a	b	Sum	Cont
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	0	1
0	1	1	0	0	1	0	1
0	1	1	1	1	0	0	1

0	1	1	1	1	0	0	1
1	0	0	0	1	0	0	1
1	0	0	1	1	0	0	1
1	0	1	0	1	0	1	0
1	0	1	1	1	0	1	0
1	1	0	0	1	1	0	0
1	1	0	1	1	1	0	0
1	1	1	0	1	1	1	0
1	1	1	1	0	0	0	1

Handwritten notes on a chalkboard, possibly representing a list or a sequence of items, with vertical lines separating columns of characters.

Handwritten notes on a chalkboard, possibly representing a list or a sequence of items, with vertical lines separating columns of characters.

